



A8.2 Circuits, expressions and truth tables

Boolean algebra and logic circuits · A level · OCR H446 1.4.3, AQA 7517

4.6.4.1, Eduqas A500QS 1.2 · about 20 min

What this lesson is about

Reading and drawing circuits, defining a problem in Boolean logic, and sum of products from a truth table.

- From circuit to expression
- From expression to circuit
- From expression to truth table
- Defining a problem with Boolean logic
- From truth table to expression: sum of products

Questions

6 marks in all

1. $Q = \neg(A \vee B) \vee (B \wedge C)$. $A = 0$, $B = 1$ and $C = 0$. What is Q ? [1 mark]

Answer: 0. $A \vee B$ is 1, so $\neg(A \vee B)$ is 0; $B \wedge C$ is 0; $0 \vee 0$ is 0.

2. For how many of the 8 input rows is $Q = \neg(A \vee B) \vee (B \wedge C)$ equal to 1? [1 mark]

Answer: 4. Rows 000, 001, 011 and 111: the NOR gives the first two and $B \wedge C$ gives the last two.

3. "The alarm sounds if the robot has bumped (K), or if it is close (C) while the battery is low (L)." Which expression matches? [1 mark]

- ☐ A $K \vee (C \wedge L)$
☐ B $(K \vee C) \wedge L$
☐ C $K \wedge C \wedge L$
☐ D $K \vee C \vee L$

Answer: A. "While" joins C and L with AND; "or" adds K on its own.

4. A truth table for A, B and C has $Q = 1$ only on the row $A=1$ $B=0$ $C=1$. Write its minterm in OCR notation, with the letters in the order A, B, C. [1 mark]

Answer: $A \wedge \neg B \wedge C$. Each input that is 0 in the row gets a NOT; the letters are joined by AND.

5. How many gates does the circuit for $(A \vee B) \wedge \neg C$ need? [1 mark]

- ☐ A 3
☐ B 2
☐ C 4
☐ D 5

Answer: A. One XOR, one NOT and one AND: one gate per operator.

6. On a circuit diagram, what does a dot where two wires meet show?

[1 mark]

- ☐ A The wires are connected (a junction)
- ☐ B The wires cross without connecting
- ☐ C A NOT gate
- ☐ D The output of the circuit

Answer: A. A junction dot means the signal splits to both wires; crossing wires without a dot are not connected.

The task: truth table to expression

Write `sum_of_products(outputs)`. Its input `outputs` is a list of eight integers, each 0 or 1: the Q column of a truth table for inputs A, B and C, with the rows in binary order, so `outputs[0]` is the row A=0 B=0 C=0 and `outputs[7]` is A=1 B=1 C=1. It returns a string: `Q =` followed by the minterms joined with `OR`. Each minterm is in brackets, lists A, B and C in that order joined with `AND`, and writes an input that is 0 in that row as `NOT` and a space before the letter. If no row is 1, it returns `Q = 0`. For example, `[0, 0, 1, 0, 0, 0, 0, 1]` gives `Q = (NOT A AND B AND NOT C) OR (A AND B AND C)`. Print the result for these three tables, one per line, in this order: `[0, 1, 1, 1, 1, 1, 1, 1]`, then `[0, 0, 1, 0, 0, 0, 1, 1]`, then `[0, 0, 0, 0, 0, 0, 0, 0]`.

```
# the two lines every program starts with: the commands, then the robot
from bugbot import *
connect()

def sum_of_products(outputs):
    return "Q = "

print(sum_of_products([0, 1, 1, 1, 1, 1, 1, 1]))
print(sum_of_products([0, 0, 1, 0, 0, 0, 1, 1]))
print(sum_of_products([0, 0, 0, 0, 0, 0, 0, 0]))
```

The hint students can ask for: Row number *i*, written as three binary digits, is the values of A, B and C on that row. For each row whose output is 1, turn each digit into a letter or NOT and a letter, join them with AND inside brackets, then join the terms with OR. Think about what to print when no row is 1.

A solution

```
# the two lines every program starts with: the commands, then the robot
from bugbot import *
connect()

def sum_of_products(outputs):
    names = ["A", "B", "C"]
    terms = []
    for i in range(8):
        if outputs[i] == 1:
            bits = format(i, "03b")
            literals = []
            for k in range(3):
                if bits[k] == "1":
                    literals.append(names[k])
                else:
                    literals.append("NOT " + names[k])
            terms.append("(" + " AND ".join(literals) + ")")
    if len(terms) == 0:
        return "Q = 0"
    return "Q = " + " OR ".join(terms)

stop_rule = [0, 1, 1, 1, 1, 1, 1, 1]
led_rule = [0, 0, 1, 0, 0, 0, 1, 1]
never = [0, 0, 0, 0, 0, 0, 0, 0]
print(sum_of_products(stop_rule))
print(sum_of_products(led_rule))
print(sum_of_products(never))
```

Any program that meets the task's checks is marked correct in the simulator; this is one way, not the only way.

BugBotLab · free Python lessons that drive a robot · www.bugbotlab.com/learn/a8-2-circuits-and-expressions/ · You may copy this for your class.