



A8.7 Half adders and full adders

Boolean algebra and logic circuits · A level · OCR H446 1.4.3, AQA 7517

4.6.4.1 · about 20 min

Name _____

Class _____

Date _____

What this lesson is about

The full adder's expressions, building it from half adders, and chaining full adders into a ripple carry adder.

- The half adder, again
- Why "half"?
- The full adder
- Two half adders and an OR gate
- Adding whole numbers: the ripple carry adder

Questions

5 marks in all

- Which expressions give a half adder's outputs? [1 mark]
 - ☐ A $S = A \vee B, C = A \wedge B$
 - ☐ B $S = A \vee B, C = A \wedge B$
 - ☐ C $S = A \wedge B, C = A \vee B$
 - ☐ D $S = A \vee B, C = A \vee B$
- Why is a half adder not enough to add multi-bit numbers? [1 mark]
 - ☐ A It has no input for the carry from the previous column
 - ☐ B It cannot add 1 and 1
 - ☐ C It has no sum output
 - ☐ D It only works on the leftmost bit
- A full adder has $A = 1, B = 0$ and $C_{in} = 1$. Give C_{out} and S as two digits, C_{out} first. [1 mark]

- How is a full adder built from half adders? [1 mark]
 - ☐ A Two half adders, with their two carry outputs joined by an OR gate
 - ☐ B Two half adders, with their carry outputs joined by an AND gate
 - ☐ C Three half adders in a row
 - ☐ D One half adder and a NOT gate

5. What does this program print?

[1 mark]

```
def full_adder(a, b, cin):
    s1, c1 = a ^ b, a & b
    return s1 ^ cin, c1 | (s1 & cin)

carry = 0
bits = ""
for a, b in [(1, 1), (1, 0), (0, 1), (1, 0)]:
    s, carry = full_adder(a, b, carry)
    bits = str(s) + bits
print(bits, carry)
```

The task: a 4-bit ripple carry adder

Write three functions. Every bit is the integer 0 or 1. - `half_adder(a, b)` returns a tuple `(sum, carry)`. - `full_adder(a, b, carry_in)` returns a tuple `(sum, carry_out)`, and must be built from two calls to `half_adder` and an OR. - `add4(x, y)` takes two strings of four characters, each "0" or "1", with the most significant bit first. It adds them with a ripple of `full_adder` calls, starting from the rightmost bit with a carry in of 0, and returns a tuple `(total, carry)`: `total` a 4-character string of the sum bits, most significant first, and `carry` the final carry out (0 or 1). Your program may not use `int()`, `bin()`, `format()` or `sum()`. For each pair `("0110", "0111")`, `("1011", "0110")`, `("1111", "0001")` and `("0101", "1010")`, in that order, print one line in exactly this form: `0110 + 0111 = 1101 carry 0`

```
# the two lines every program starts with: the commands, then the robot
from bugbot import *
connect()

def half_adder(a, b):
    return 0, 0

def full_adder(a, b, carry_in):
    return 0, 0

def add4(x, y):
    return "0000", 0
```

Plan your program here, then type it in and press Run.



Do it on the robot

www.bugbotlab.com/learn/a8-7-half-and-full-adders/

The simulator checks it and tells you when it passes. Nothing to install, no account.

Challenges

1. Change `add4` to add numbers of any length, and add two 8-bit numbers.
2. Count the gates in your 4-bit adder, counting XOR, AND and OR as one gate each.
3. Two's complement subtraction A minus B is A plus (NOT B) plus 1. Use your adder with a carry in of 1 to subtract 0011 from 0110.