



F9.2 Logic circuits and expressions

Logic and computer systems · GCSE · OCR J277 2.4.1, AQA 8525 3.4.2,
Edexcel 1CP2 1.3.1 · about 15 min

What this lesson is about

Combining gates, Boolean expressions, XOR, and the half adder.

- A circuit and its expression
- XOR
- Adding two bits
- From a problem to a circuit

Questions

6 marks in all

1. In $Q = (A \text{ AND } B) \text{ OR } (\text{NOT } C)$, $A = 0$, $B = 1$ and $C = 1$. What is Q ? [1 mark]

Answer: 0. $A \text{ AND } B$ is 0, $\text{NOT } C$ is 0, and $0 \text{ OR } 0$ is 0.

2. In $Q = (A \text{ AND } B) \text{ OR } (\text{NOT } C)$, $A = 0$, $B = 0$ and $C = 0$. What is Q ? [1 mark]

Answer: 1. $\text{NOT } C$ is 1, so the OR gives 1.

3. When does XOR output 1? [1 mark]

- ☐ A When the inputs are different
☐ B When both inputs are 1
☐ C When at least one input is 1
☐ D When both inputs are 0

Answer: A. Exclusive OR: one or the other, but not both.

4. In a half adder, which gate gives the carry bit? [1 mark]

- ☐ A AND
☐ B XOR
☐ C OR
☐ D NOT

Answer: A. The carry is 1 only when both bits are 1.

5. What does this program print? [1 mark]

```
def XOR(a, b): return 1 if a != b else 0
for a, b in [(1, 1), (1, 0)]:
    print(a & b, XOR(a, b))
```

Answer:

```
1 0
0 1
```

1 + 1 is carry 1, sum 0; 1 + 0 is carry 0, sum 1.

6. "Beep if the robot is close and moving, or it has bumped." Which expression matches?

[1 mark]

- ☐ A (close AND moving) OR bumped
- ☐ B close AND (moving OR bumped)
- ☐ C (close OR moving) AND bumped
- ☐ D NOT close AND moving AND bumped

Answer: A. The and joins close and moving; the or adds bumped on its own.

The task: a half adder

Write `AND(a, b)` and `XOR(a, b)` as functions of 0s and 1s. XOR must be built from AND, OR and NOT functions you also write, as `(A OR B) AND NOT (A AND B)`, not with `!=`. Print the half adder's truth table as four lines in the form `A=1 B=1 carry=1 sum=0`.

```
# the two lines every program starts with: the commands, then the robot
from bugbot import *
connect()

def AND(a, b): return 1 if a and b else 0
def OR(a, b): return 1 if a or b else 0
def NOT(a): return 1 - a
```

The hint students can ask for: XOR is true when the inputs differ, which is the same as saying at least one is true but not both: build it from OR, AND and NOT. The carry is the plain AND of the inputs.

A solution

```
from bugbot import *
connect()
def AND(a, b):
    return 1 if a == 1 and b == 1 else 0

def OR(a, b):
    return 1 if a == 1 or b == 1 else 0

def NOT(a):
    return 1 - a

def XOR(a, b):
    return AND(OR(a, b), NOT(AND(a, b)))

for a in [0, 1]:
    for b in [0, 1]:
        print(f"A={a} B={b} carry={AND(a, b)} sum={XOR(a, b)}")
```

Any program that meets the task's checks is marked correct in the simulator; this is one way, not the only way.